 


Processor Design – Single Cycle Processor

Hung-Wei Tseng

Recap: the stored-program computer

- Store instructions in memory
- The program counter (PC) controls the execution



How many of these?

Instruction Count!

How long is it take to execution each of these?

Cycles per instruction * cycle time

Recap: Performance Equation

$$\text{Execution Time} = \frac{\text{Instructions}}{\text{Program}} \times \frac{\text{Cycles}}{\text{Instruction}} \times \frac{\text{Seconds}}{\text{Cycle}}$$


- $ET = IC * CPI * \text{Cycle Time}$
- IC (Instruction Count)
 - **ISA**, **compiler**, algorithm, programming language, **programmer**
- CPI (Cycles Per Instruction)
 - **Machine implementation**, microarchitecture, **compiler**, application, algorithm, programming language, **programmer**
- Cycle Time (Seconds Per Cycle)
 - Process technology, **microarchitecture, ISA**, **programmer**

We demonstrated these
We learned about this


We will be talking about this!

Recap: MIPS ISA


- R-type: add, sub, and etc...

 

- I-type: addi, lw, sw, beq, and etc...

 


- J-type: j, jal, and etc...

 

Recap from CSE140: Clock

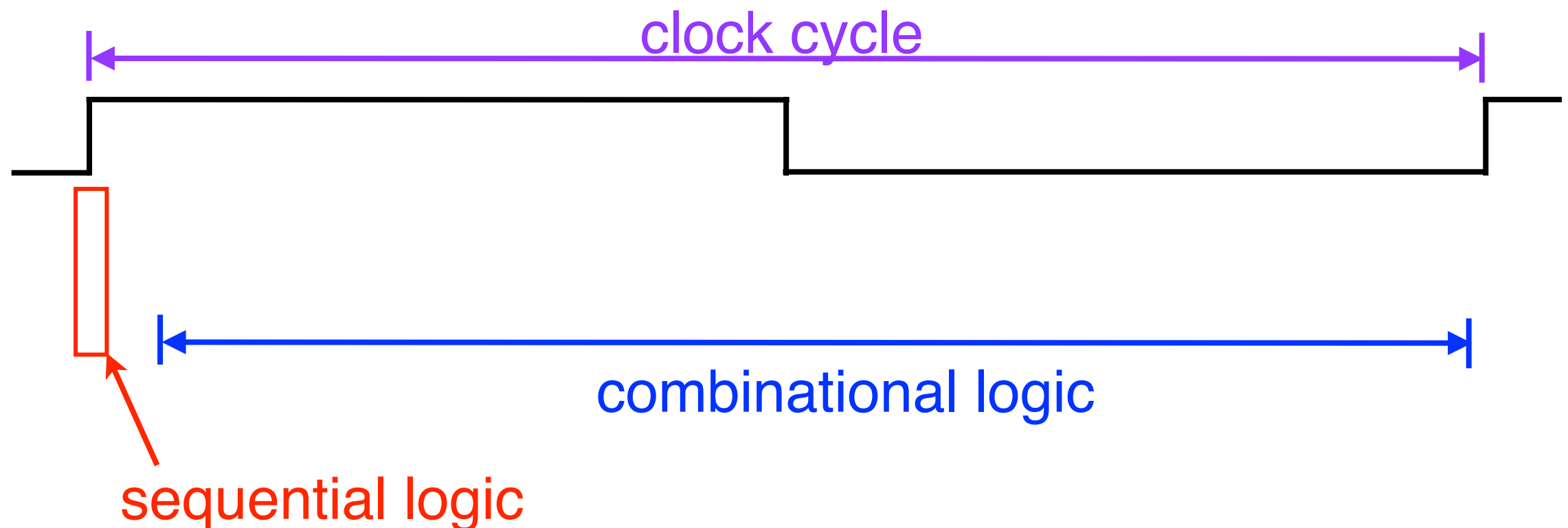- A hardware signal defines when data is valid and stable
 - Think about the clock in real life!
- We use edge-triggered clocking
 - Values stored in the sequential logic is updated only on a clock edge



Announcement

- Reading quizzes for 4.5-4.9 due tomorrow
- No new reading quizzes until midterm (oh! yeah~~~)
- Homework 2 due next Monday

Outline


- Implementing a Single-cycle MIPS processor

Designing a simple MIPS processor

- Support MIPS ISA in hardware
 - Design the datapath: add and connect all the required elements in the right order
 - Design the control path: control each datapath element to function correctly.
- Starts from designing a single cycle processor
 - Each instruction takes exactly one cycle to execute


Basic steps of execution

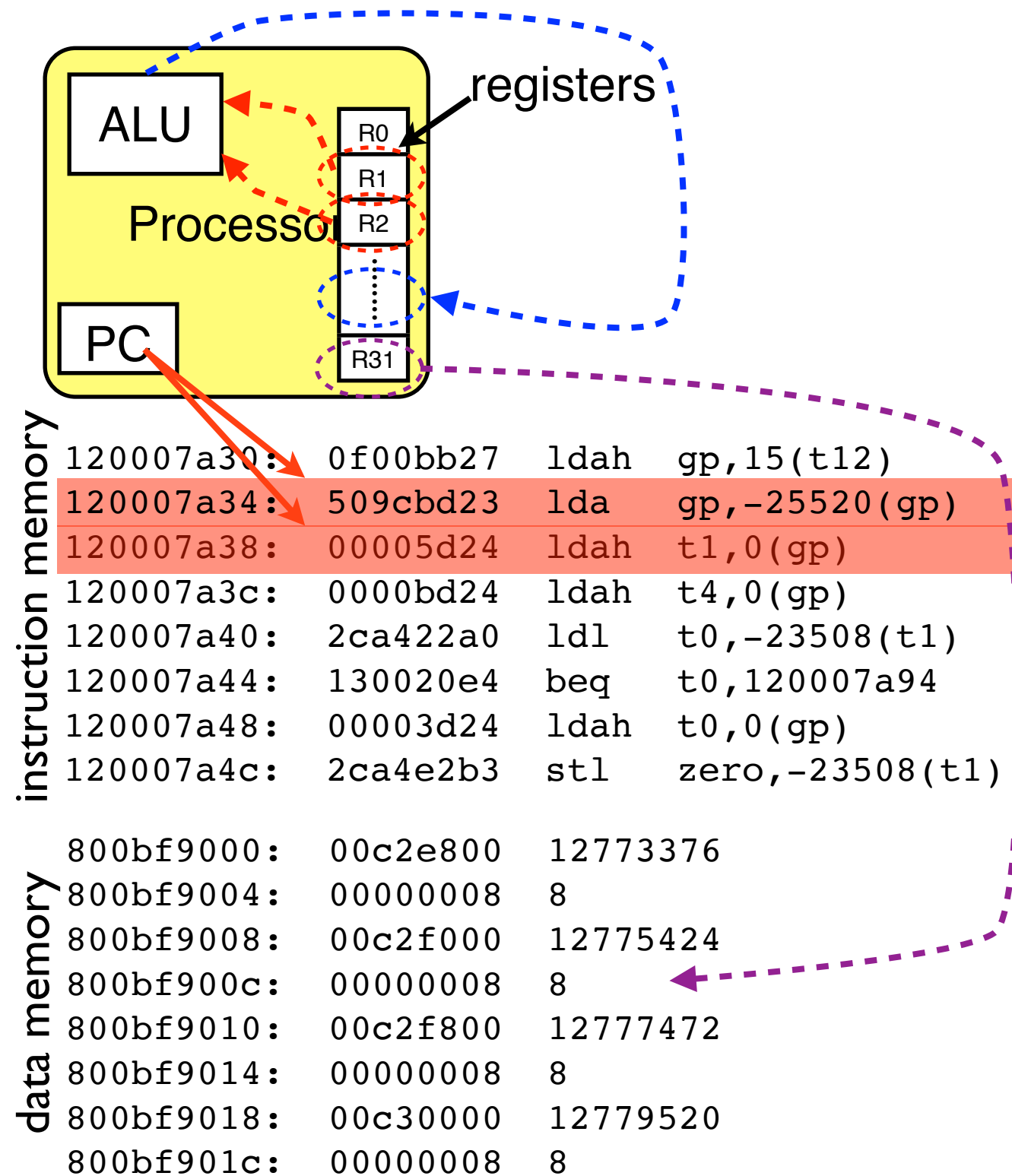- Instruction fetch: where?
instruction memory
- Decode:
 - What's the instruction?
 - Where are the operands?
registers
- Execute **ALUs**
- Memory access
 - Where is my data?
data memory
- Write back
 - Where to put the result
registers
- Determine the next PC




Recap: MIPS ISA


- R-type: add, sub, and etc...

 

- I-type: addi, lw, sw, beq, and etc...

 

- J-type: j, jal, and etc...

 

Implementing an R-type instruction

- How many of the following datapath elements is necessary for an R-type instruction?

I. Instruction Memory

II. Data memory

III. Register file

IV. Program counter

V. ALU

A. 1

B. 2

C. 3


D. 4

E. 5

instruction = MEM[PC]

REG[rd] = REG[rs] op REG[rt]

PC = PC + 4

 


Implementing an R-type instruction

- What's right order of accessing the datapath elements for an R-type instruction? (only count the first time touching it)
 - I. Instruction Memory
 - II. Data memory
 - III. Register file
 - IV. Program counter
 - V. ALU
 - A. I, III, V, IV
 - B. IV, I, III, V**
 - C. I, V, III, IV
 - D. IV, V, I, III
 - E. none of the above

Implementing an R-type instruction



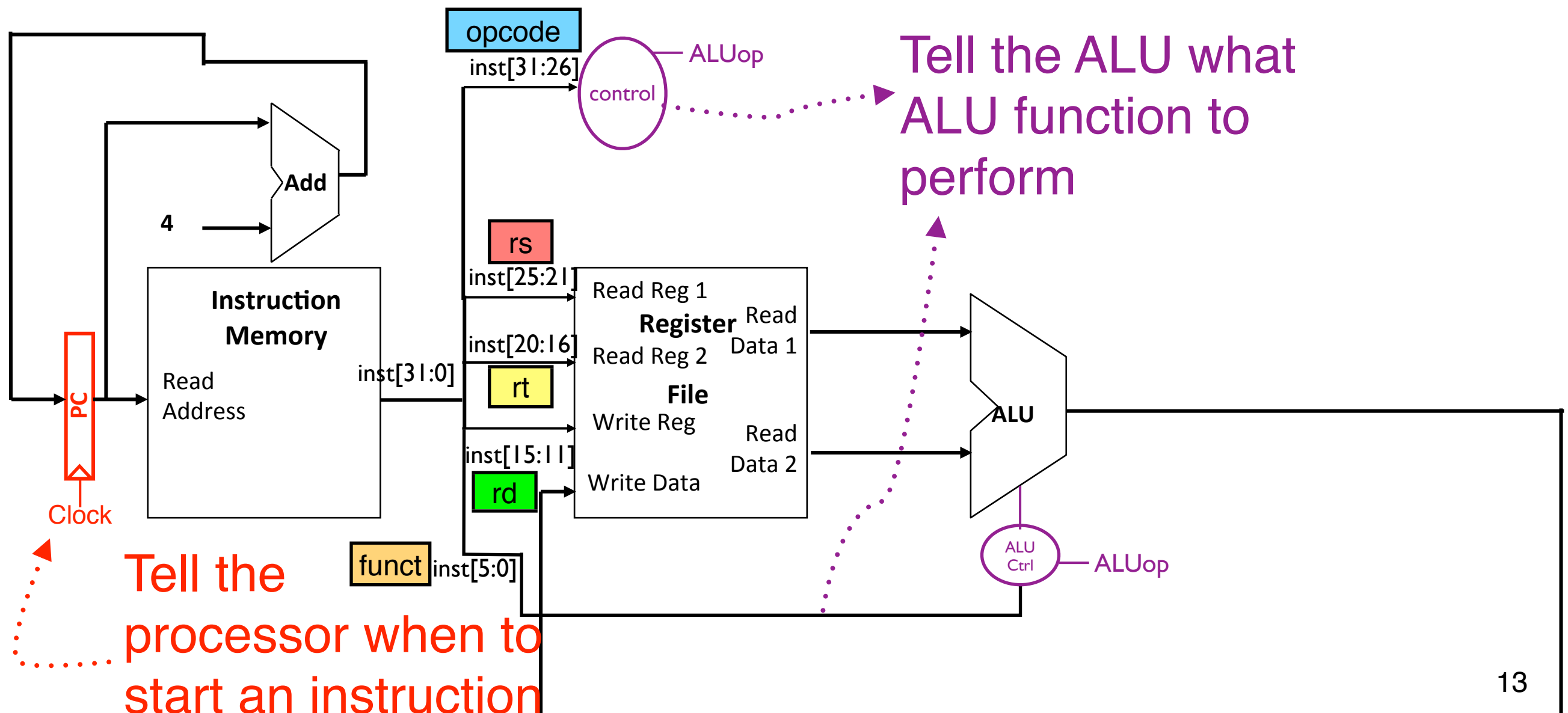instruction = MEM[PC]
REG[rd] = REG[rs] op REG[rt]
PC = PC + 4



Implementing a load instruction

- How many of the following datapath elements is necessary for a load instruction?

I. Instruction Memory

II. Data memory

III. Register file

IV. Program counter

V. ALU

A. 1

B. 2

C. 3


D. 4

E. 5

instruction = MEM[PC]

REG[rt] = MEM[signext(immediate) +
REG[rs]]

PC = PC + 4

 

Implementing a load instruction

- What's right order of accessing the datapath elements for a load instruction? (only count the first time touching it)
 - I. Instruction Memory
 - II. Data memory
 - III. Register file
 - IV. Program counter
 - V. ALU

A. IV, I, III, V, II


B. IV, I, III, II, V

C. IV, I, V, II, III

D. IV, I, II, V, III

E. none of the above

Implementing a load instruction

 

instruction = MEM[PC]

REG[rt] = MEM[signext(immediate) + REG[rs]]


PC = PC + 4

Set different control signals for different types of instructions

Set to 1 if it's a load

Set to 1 if it's a load

Set to 0 if it's a load

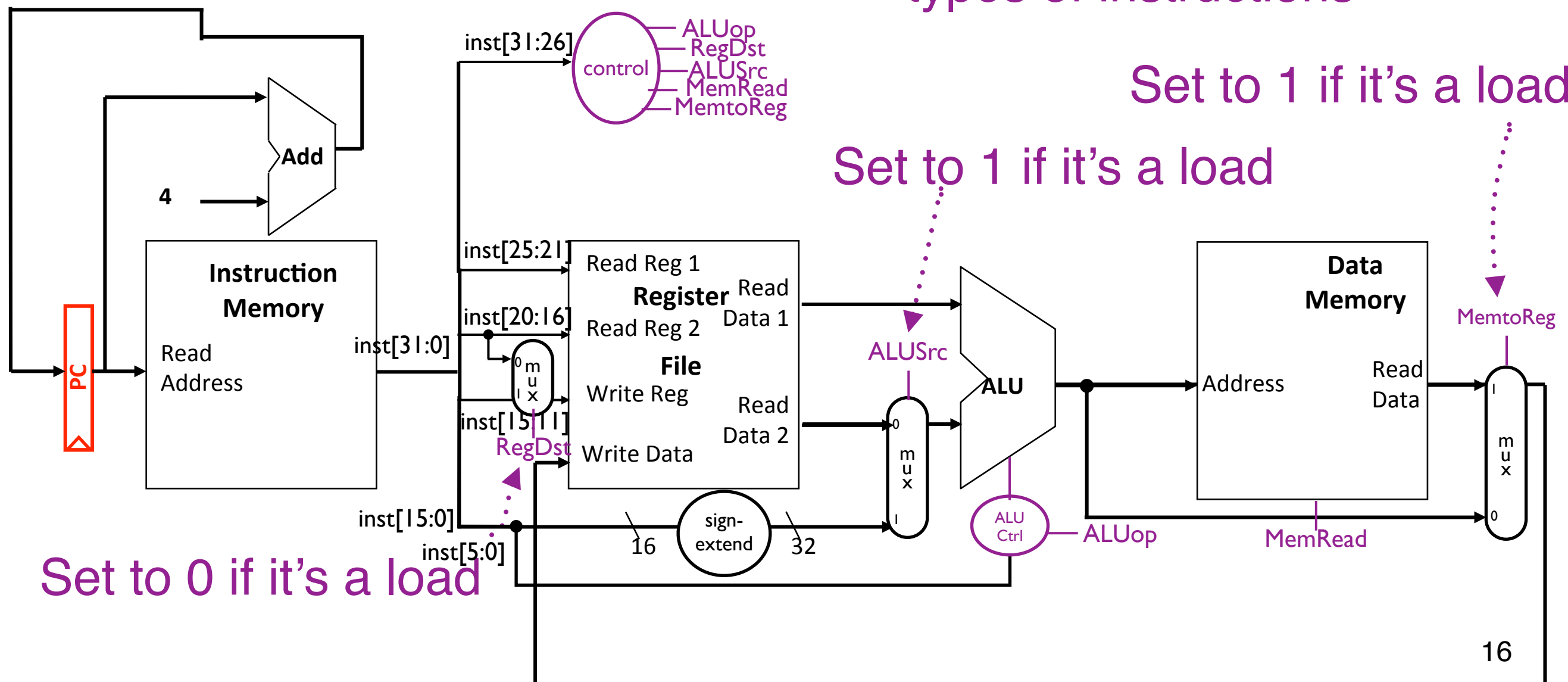

Implementing a store instruction

- How many of the following datapath elements is necessary for a store instruction?

I. Instruction Memory

II. Data memory

III. Register file

IV. Program counter

V. ALU

A. 1

B. 2

C. 3


D. 4

E. 5

instruction = MEM[PC]

$\text{MEM}[\text{signext}(\text{immediate}) + \text{REG}[\text{rs}]] = \text{REG}[\text{rt}]$

$\text{PC} = \text{PC} + 4$

 

Implementing a store instruction

- What's right order of accessing the datapath elements for a store instruction? (only count the first time touching it)
 - I. Instruction Memory
 - II. Data memory
 - III. Register file
 - IV. Program counter
 - V. ALU
 - A. IV, I, III, V, II
 - B. IV, I, III, II, V
 - C. IV, I, V, II, III
 - D. IV, I, II, V, III
 - E. none of the above

Implementing a store instruction

6 bits

5 bits

5 bits

16 bits

opcode

rs


rt

immediate / offset

instruction = MEM[PC]

MEM[signext(immediate) + REG[rs]] = REG[rt]

PC = PC + 4

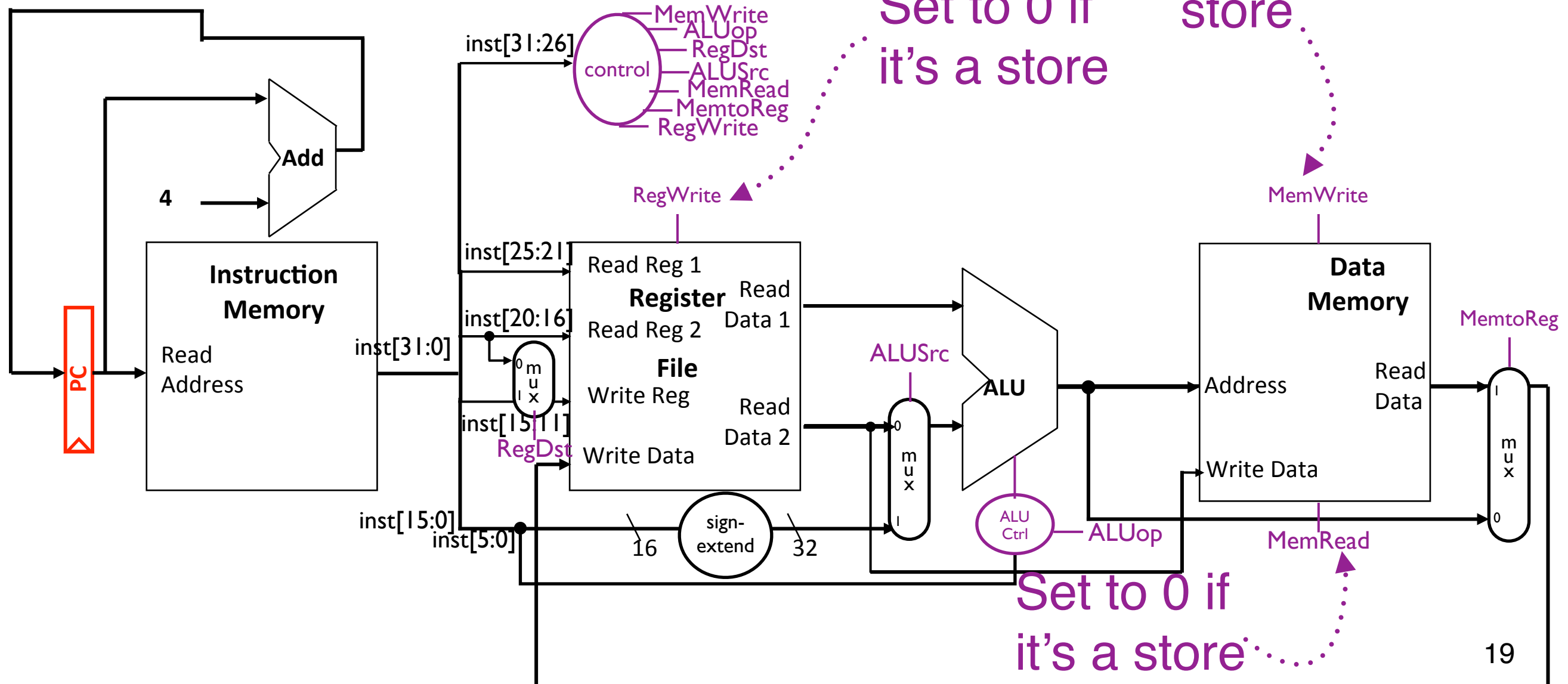

Implementing a branch instruction

- How many of the following datapath elements is necessary for a branch instruction?

I. Instruction Memory

II. Data memory

III. Register file

IV. Program counter

V. ALU

A. 1

B. 2


C. 3

D. 4

 E. 5

instruction = MEM[PC]

PC = (REG[rs] == REG[rt]) ? PC + 4 + SignExtImmediate * 4 : PC + 4




Implementing a branch instruction



instruction = MEM[PC]

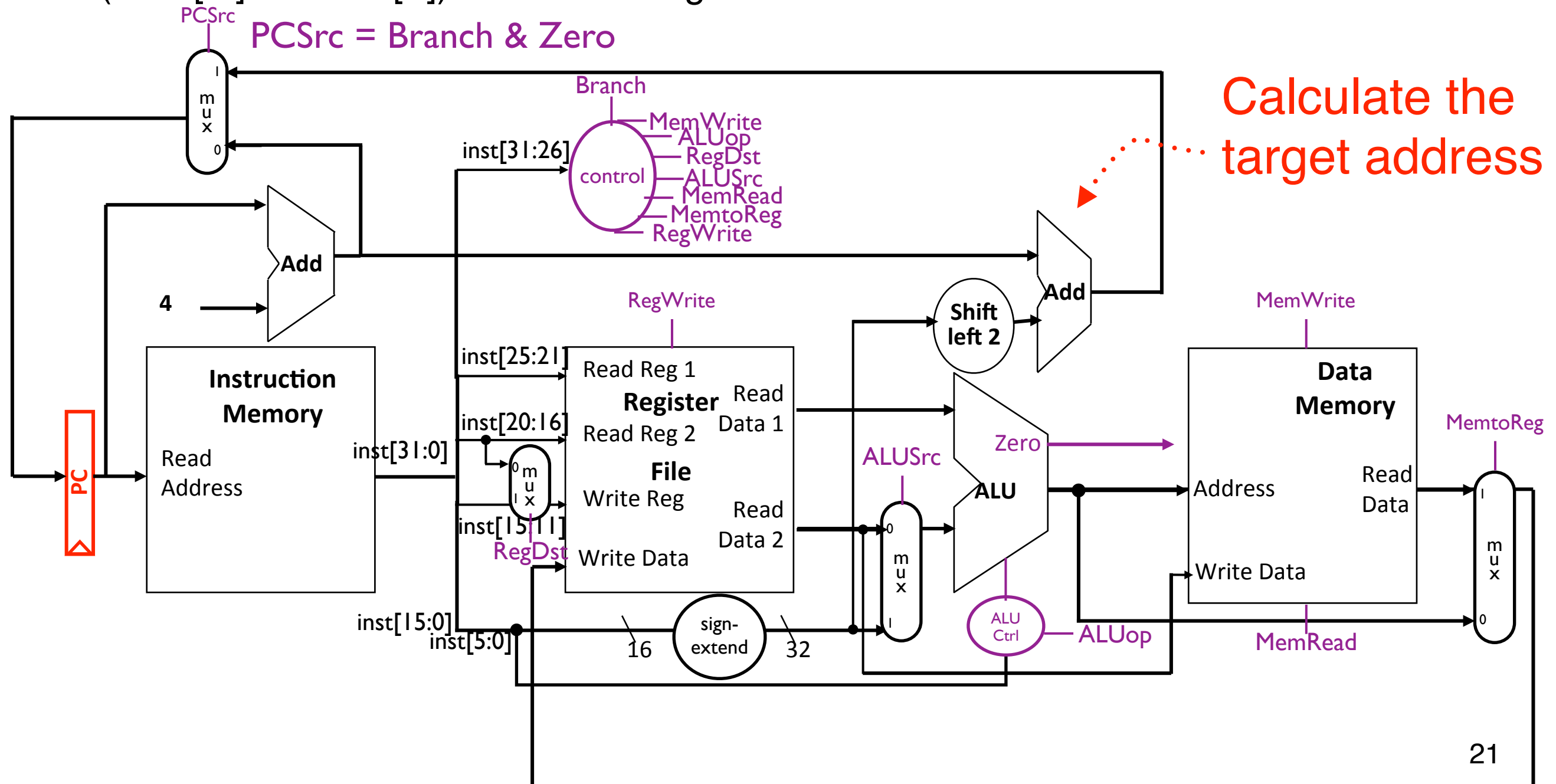
PC = (REG[rs] == REG[rt]) ? PC + 4 + SignExtImmediate * 4 : PC + 4



Performance of a single-cycle processor

- How many of the following statements about a single-cycle processor is correct?
 - The CPI of a single-cycle processor is always **1**
 - If the single-cycle implements lw, sw, beq, and add instructions, the sw instruction determines the cycle time
 - Hardware elements are mostly idle during a cycle
 - We can always reduce the cycle time of a single-cycle processor by supporting fewer instructions
- A. 0
- B. 1
- C. 2**
- D. 3
- E. 4

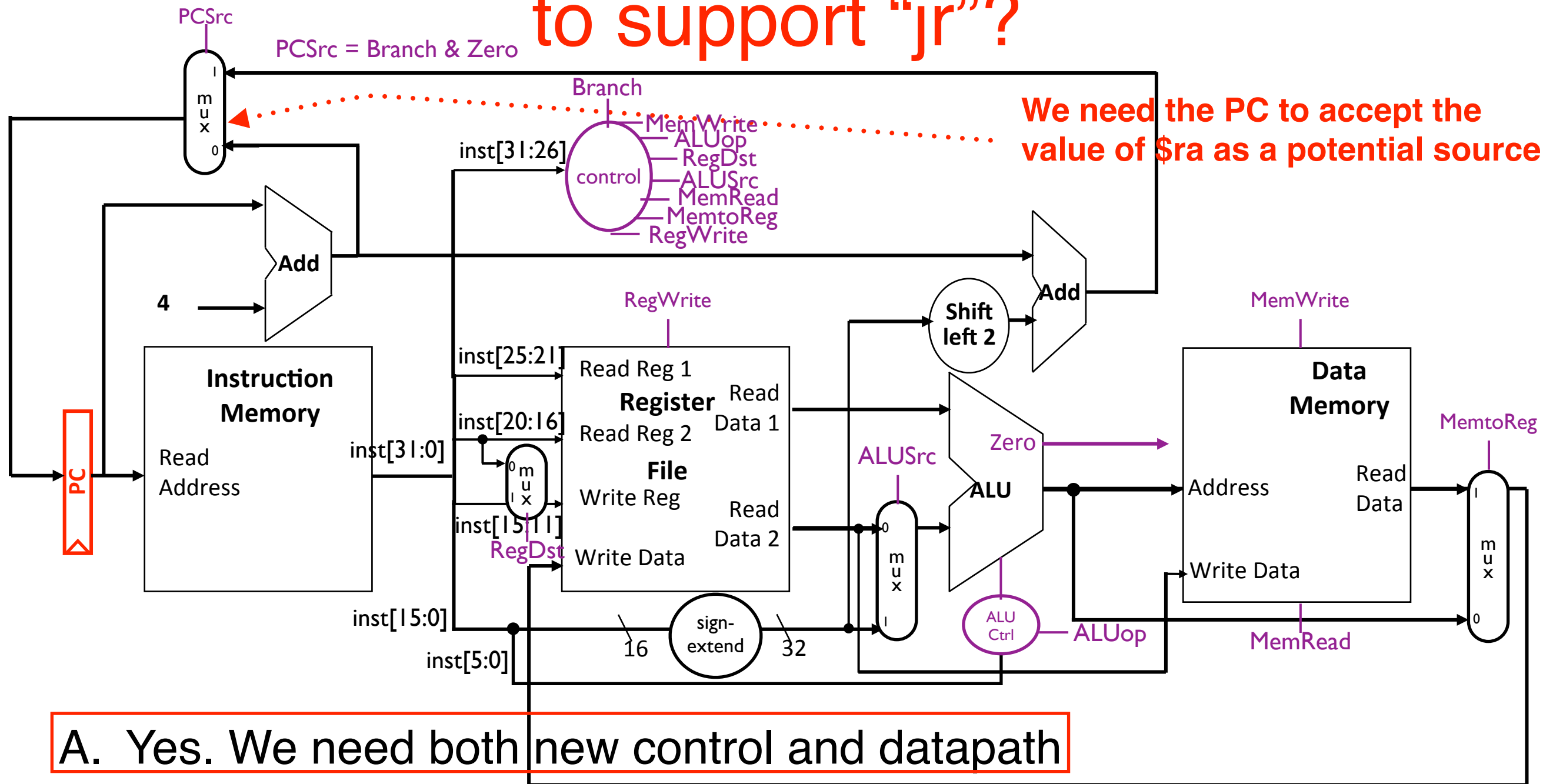Do we need to modify the current processor to support “jr”?



- B. Yes. We only need to modify datapath
- C. No. But we should modify for better performance
- D. No. Just changing the control signals is fine
- E. Single cycle cannot do jump register

Q & A